

NAME: GIELO MAR R. BANDOY
COURSE/YR: BSCpE – 3A
SUBJECT: CPE 366 – INTRO TO HDL

SYNCHRONOUS BINARY UP COUNTER

VHDL CODE FOR SYNCHRONOUS BINARY UP COUNTER:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity synbicount is
Port (rs,clk: in STD_LOGIC;
q: inout STD_LOGIC_VECTOR (3 downto 0));
end synbicount;

architecture Behavioral of synbicount is
signal div:std_logic_vector(22 downto 0);
signal temp:STD_LOGIC_VECTOR (3 downto 0);
signal clkd:std_logic;
begin
process(clk)
begin
if rising_edge(clk)then
div<= div+1;
end if;
end process;
clkd<=div(22);
process(clkd)
begin
```


```

if(clkd='1' and clkd'event) then
if(rs='1') then temp<=(others=>'0');
else temp<=temp+1;
end if;
q<= temp;
end if;
end process;
end Behavioral;

```

TRUTH TABLE:

3-bit Asynchronous up counter			
Clock	QC	QB	QA
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0
9	0	0	1

 

RTL VIEWER:

