

NAME: GIELO MAR R. BANDOY
COURSE/YR: BSCpE – 3A
SUBJECT: CPE 366 – INTRO TO HDL

BCD UP COUNTER

VHDL CODE OF BCD UP COUNTER:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity bcdupcount is
Port ( clk,rs : in  STD_LOGIC;
      q : inout  STD_LOGIC_VECTOR (3 downto 0));
end bcdupcount;

architecture Behavioral of bcdupcount is
signal div:std_logic_vector(22 downto 0);
signal clkd:std_logic;

begin

process(clkd)
begin
if rising_edge(clk)then
div<= div+1;
end if;
end process;

clkd<=div(22);

process(clkd,rs)
begin
if rs='0' or q="1010" then
q<="0000";
```

```
elsif clkd'event and clkd='1' then
```

```
q<=q+1;
```

```
end if;
```

```
end process;
```

```
q<=q;
```

```
end Behavioral;
```

TRUTH TABLE OF BCD UP COUNTER:

Clock	QD	QC	QB	QA
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	0	0	0	0

NETLIST VIEWER:

